


# Chapter 18

## Current, Resistance & Power



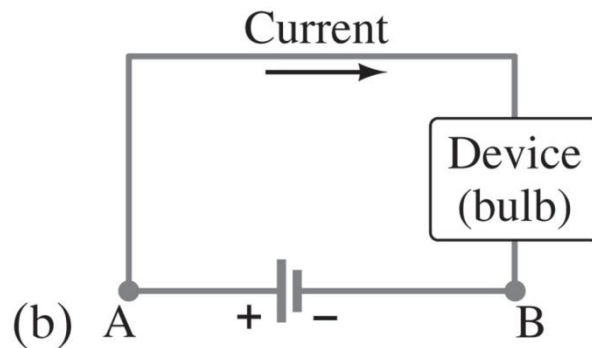
# Electric Current & Circuits

- 3 things necessary for electric current to flow at a useable rate through a circuit
  1. Source of potential difference (increase)
    - battery
  2. Closed loop conducting pathway
    - connecting wires
  3. Potential downhill (decrease)
    - resistor





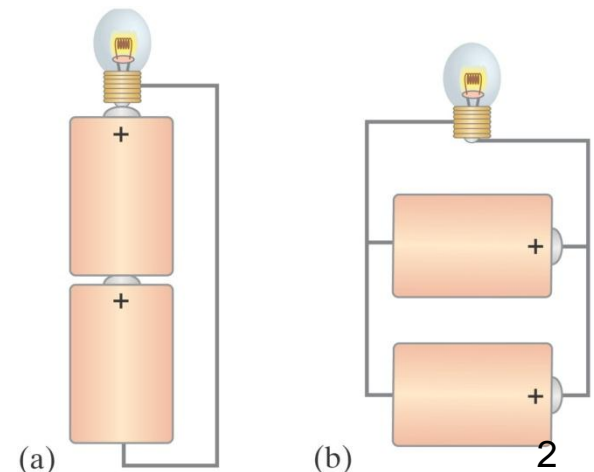Copyright © 2005 Pearson Prentice Hall, Inc.



Copyright © 2005 Pearson Prentice Hall, Inc.

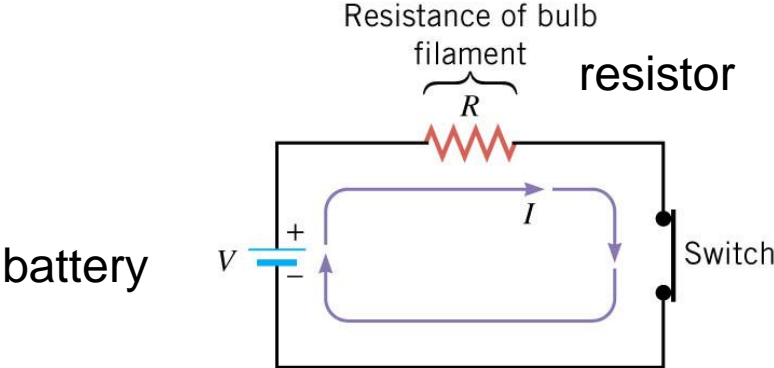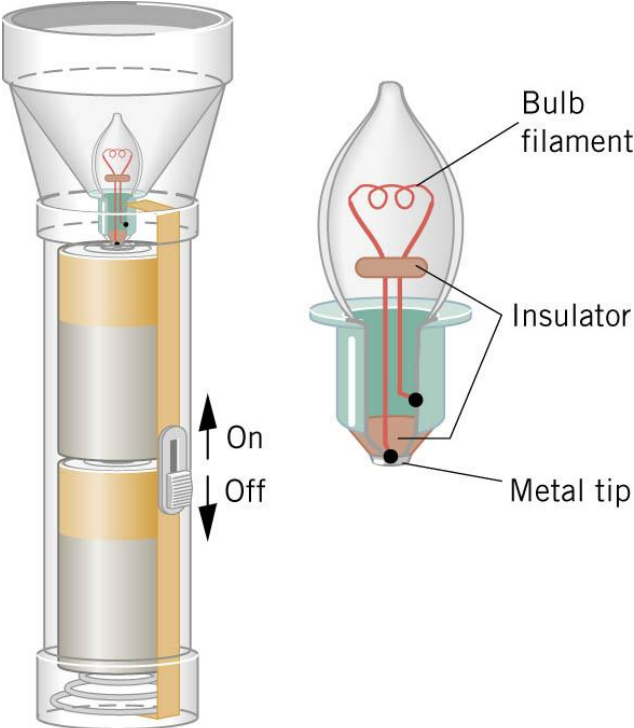You need to be able to read and draw circuit diagrams and identify direction of current flow



# Voltage (potential increase) source


- battery or power supply
- “charge pump” does work on charges supplying them with electric potential energy
- creates a potential difference ( $\Delta V$ )
  - higher potential (V) at +, lower potential at – terminal
- current flow through circuit results
- does NOT supply charge carriers
  - where are they?

# Electric Current

- number of + charge carriers passing through a cross-sectional area per second


$$I = \frac{\Delta q}{\Delta t} \quad \text{Units: } \frac{1 \text{ coulomb}}{1 \text{ second}} = 1 \text{ Ampere (A)}$$

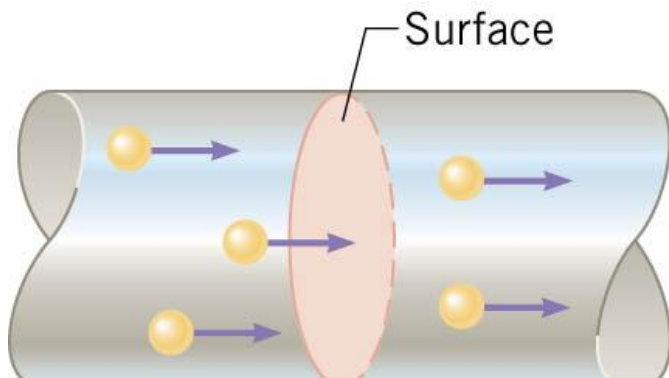- not velocity of charge carriers – water flow through pipe or hose is good equivalent




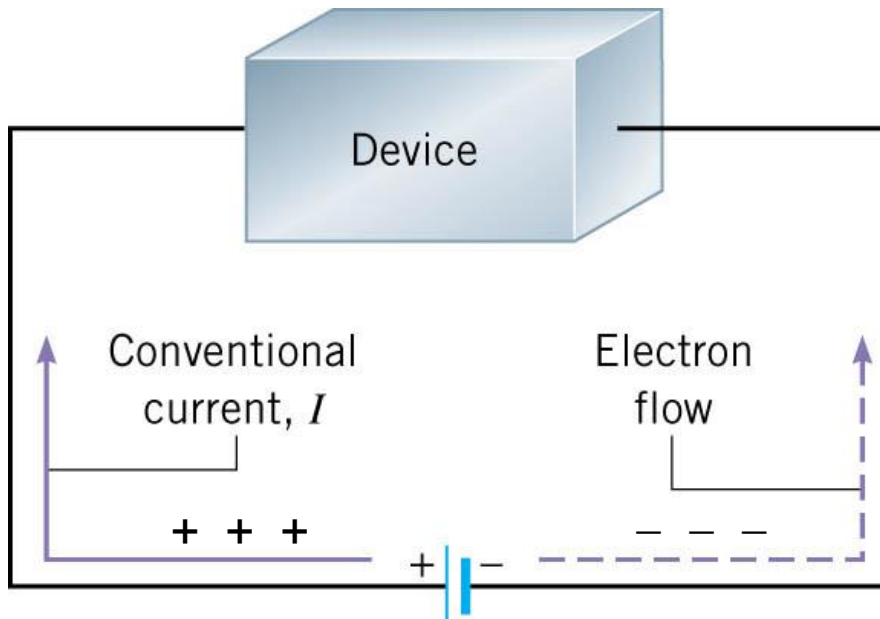
# Electric Current

- conventional current = movement of + charge carriers
- electrons actually move through wires


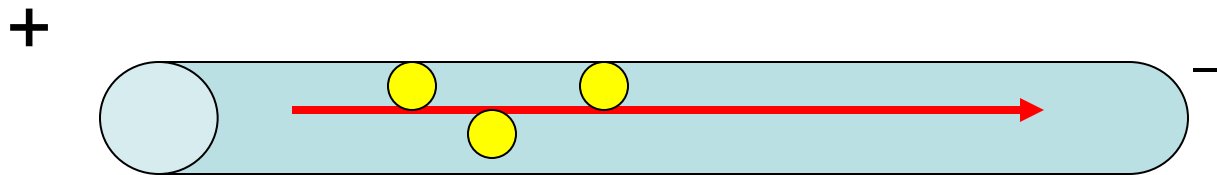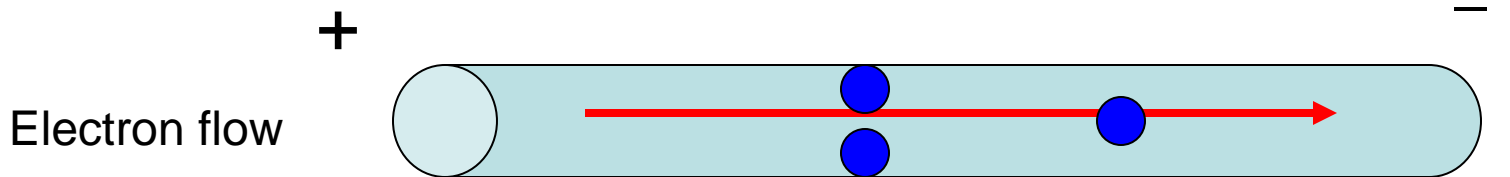
# Conventional current


What could be done to increase the flow of charges through the conductor?



Conventional current
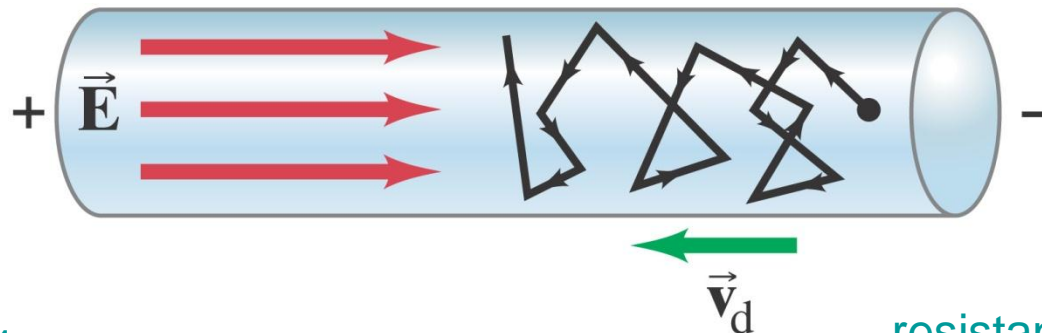
# Electrical Resistance

- impedance or opposition to the flow of electric charge by the conductor that the current is moving through
- “electrical friction”
- all conductors have resistance
  - electrons contacting atoms in metal





# Ohm's Law


- definition of resistance

$$R = \frac{V}{I} \quad \text{Units:} \quad \frac{1 \text{ Volt}}{1 \text{ Ampere}} = 1 \text{ ohm } (\Omega)$$

- what does resistance depend on?
- this ratio is constant for resistors that obey Ohm's Law,; resistance is independent of voltage and current

graph of voltage vs current is linear

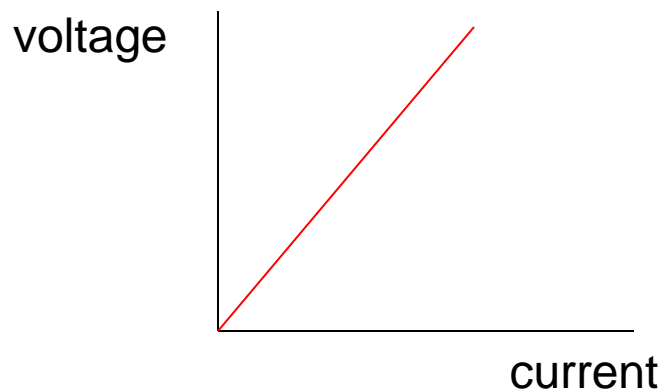
greater potential difference causes increased current



# Resistance depends on

- material property called resistivity  $\rho$
- length of conductor  $L$
- cross sectional area  $A$

$$R = \rho \frac{L}{A}$$

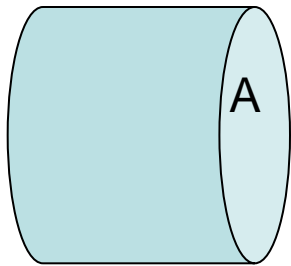

L  
short and wide =  
low resistance



long and narrow =  
high resistance

capacitor  $C=Q/V$  was definition; capacitance depended on  $A, d$

# Current Control

- 2 ways to increase current


$$I = \frac{V}{R}$$

- increase voltage (greater potential difference supplying more energy to charge carriers)
- decrease resistance by changing length, area

# Resistors

- Electrical circuit element with purpose to
  - regulate current flow
  - create a potential “downhill”
    - decrease in potential
  - take energy (potential) out of the charge carriers that flow through resistor
- Resistors do NOT take charge carriers out of the circuit
- Baseboard hot water heating system in house

# Voltage drop across resistor

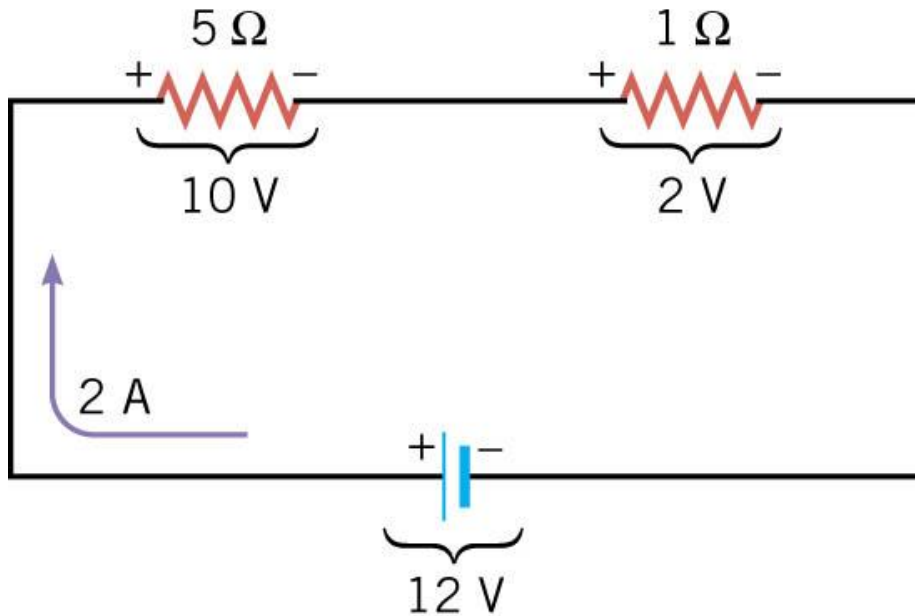

When current flows through a resistor there is a voltage decrease according to  $V=IR$

2 Amperes of current flow through both resistors


$$V_1 = (2A)(5\Omega) = 10 \text{ Volts of potential decrease}$$

$$V_2 = (2A)(1 \Omega) = 2 \text{ Volts of voltage drop}$$

Total potential increase from battery (12V) = total voltage drop from R's = 12 V

Voltage drop is due to the electrical energy usage by the device or resistor

# 3 ways to use Ohm's Law expression

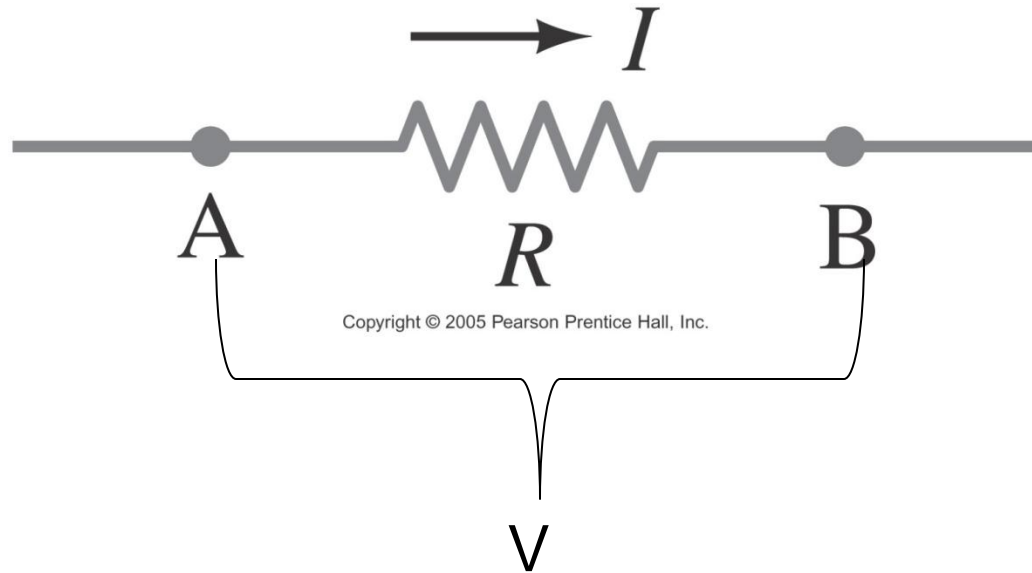

1)  $I = V/R$  to calculate current

2)  $R = V/I$  to calculate resistance of resistor

3)  $V = IR$  to calculate either

- voltage drop when current flows through resistor
- voltage required to cause current flow through resistor

# Power

$$\textit{Work} = \textit{change in energy} = q \bullet \Delta V$$

$$\textit{Power} = \frac{\textit{Work}}{\textit{time}} = \frac{\textit{energy transfer}}{\textit{time}} = \frac{q \bullet \Delta V}{t}$$

$$\textit{Power} = I \bullet V \quad \text{Units} = \text{Watts}$$

alternative expressions based on substituting Ohm's Law  $V=IR$  or  $I=V/R$

$$P = I \bullet IR = I^2 R$$

$$P = \frac{V}{R} \bullet V = \frac{V^2}{R}$$

# Energy Transfer Rate

- Watt = Joules of energy used per second
- Energy used (J) = Power • time

$$\text{Joules} = \frac{\text{Joules}}{\text{second}} \times \text{seconds}$$




# Electrical Power


- Heating of resistor or brightness of bulb is result of taking EPE from charge carriers in current
- Resistors use (dissipate) electrical energy at a certain rate = power
- Rate of energy transfer
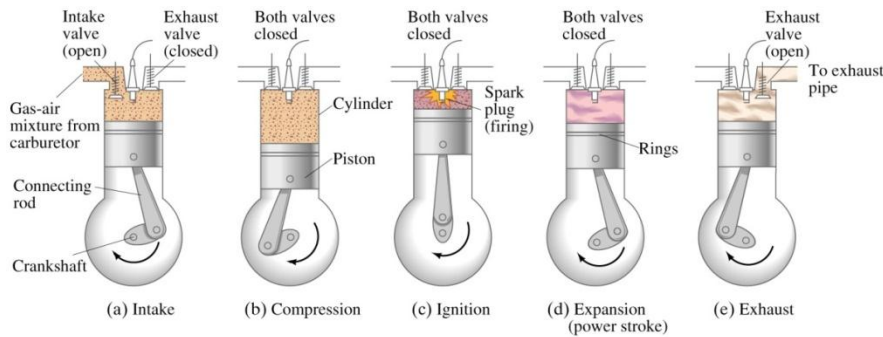
# Efficiency of a heat engine or electrical device

$$\text{efficiency } e = \frac{\text{power output}}{\text{power input}} = \frac{\text{work output}}{\text{energy input}}$$



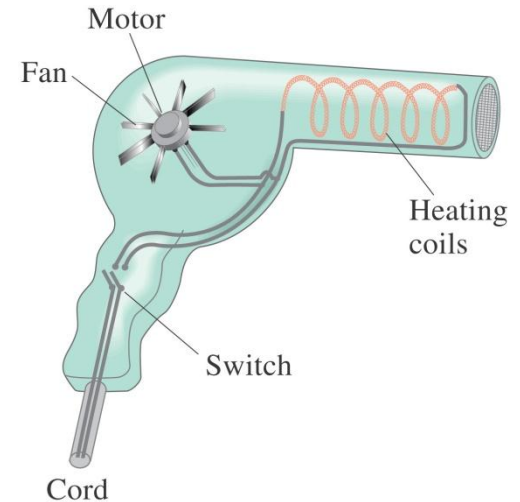Copyright © 2005 Pearson Prentice Hall, Inc.



Copyright © 2005 Pearson Prentice Hall, Inc.

all devices and machines are less than 100% efficient